

B.Sc. Part-2 Physics (Hons) Paper-iv, Lecture-16 on the topic


“Kirchhoff's Laws and Mesh Current Analysis.”

Dr. Mohammad Arslan, Dept. of Physics  
B.Sc. Part-2, Physics (Hons), Paper-IV<sup>th</sup>  
Lecture-16

\* Kirchhoff's Laws  $\Rightarrow$

① Kirchhoff's ~~current~~ current law  $\Rightarrow$

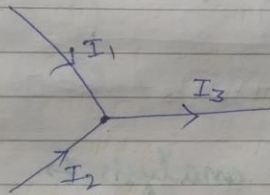Kirchhoff's current law states that current flowing into a node or a junction must be equal to current flowing out of it. This is a consequence of charge conservation.



The current in the three wires must be related by:


$$I_1 + I_2 = I_3$$

It is important to note that the current flowing towards the junction are taken to be positive, and the current flowing away from the junction is taken negative, i.e.

$$I_1 + I_2 + (-I_3) = 0$$

② Kirchhoff's voltage law  $\Rightarrow$

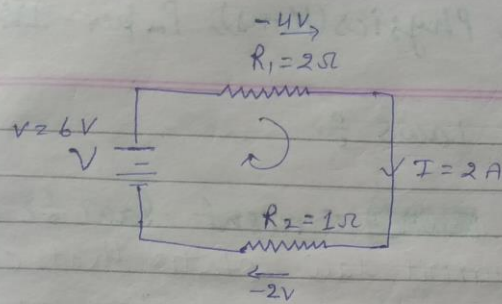Kirchhoff's voltage law states that the sum of voltages around any closed loop in a circuit must be equal to zero. This is a consequence of energy conservation.




In any loop containing any number of components Kirchhoff's voltage law can be written as

$$\sum_{k=1}^n V_k = 0$$

i.e.  $V_1 + V_2 + V_3 + \dots = 0$
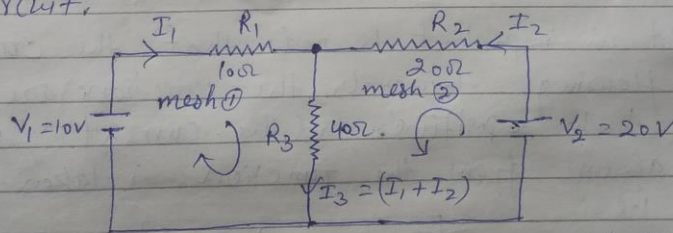
### Mesh current analysis $\Rightarrow$

mesh current analysis is a technique used to find the current circulating around a loop or mesh within any closed path of a circuit.



To analyse the circuit using Kirchhoff's current law equations to determine the current  $I_1$  and  $I_2$  flowing in the two resistors.

apply Kirchhoff's voltage law in mesh (1)

$$V_1 = I_1 R_1 + I_3 R_3$$

$$V_1 = I_1 R_1 + (I_1 + I_2) R_3$$



$$V_1 = I_1 R_1 + I_1 R_3 + I_2 R_3$$

$$V_1 = I_1 (R_1 + R_3) + I_2 R_3 \quad \text{--- (I)}$$

In mesh (2)

$$V_2 = I_2 R_2 + I_3 R_3$$

$$V_2 = I_2 R_2 + (I_1 + I_2) R_3$$

$$V_2 = I_2 R_2 + I_1 R_3 + I_2 R_3$$

$$V_2 = I_1 R_3 + I_2 (R_2 + R_3) \quad \text{--- (II)}$$

Now multiply by  $R_3$  in equation (I) and multiply by  $(R_1 + R_3)$  in equation (II) and subtract them

$$V_1 R_3 = I_1 R_3 (R_1 + R_3) + I_2 R_3^2$$

$$V_2 (R_1 + R_3) = I_1 R_3 (R_1 + R_3) + I_2 (R_2 + R_3) (R_1 + R_3)$$

$$V_1 R_3 - V_2 (R_1 + R_3) = I_2 [R_3^2 - (R_2 + R_3) (R_1 + R_3)]$$

$$I_2 = \frac{V_1 R_3 - V_2 (R_1 + R_3)}{[R_3^2 - (R_2 + R_3) (R_1 + R_3)]}$$

Now for  $I_1$

$$V_1 = I_1 (R_1 + R_3) + I_2 R_3$$

$$I_1 = \frac{V_1 - I_2 R_3}{(R_1 + R_3)}$$

$$I_1 = \frac{V_1}{(R_1 + R_3)} - \frac{I_2 R_3}{(R_1 + R_3)}$$

(4)

$$I_1 = \frac{V_1}{R_1 + R_3} - \frac{V_1 R_3 - V_2 (R_1 + R_3)}{[R_3^2 - (R_1 + R_3)(R_2 + R_3)]} \times \frac{R_3}{(R_1 + R_3)}$$

$$I_1 = \frac{V_1}{(R_1 + R_3)} - \frac{V_1 R_3^2 - V_2 R_3 (R_1 + R_3)}{R_3^2 (R_1 + R_3) - (R_1 + R_3)^2 (R_2 + R_3)}$$

and

$$I_3 = I_1 + I_2$$

put the values of  $V_1, V_2, R_1, R_2$  and  $R_3$   
we can find the values of  $I_1, I_2$  and  $I_3$ .