

B.Sc. Part-2 Physics (Hons) Paper-iv, Lecture-17 on the topic

“Nodal Voltage Analysis and Duality in Network.”


Dr. Mohammad Aslam, Dept. of Physics  
B.Sc. Part-2, physics (Hons), Paper-IV,  
Lecture-17

(1)

\* Nodal voltage Analysis :->

Nodal voltage analysis is used to find the unknown voltage drops around a circuit between different nodes that provide a common connection for two or more circuit components.

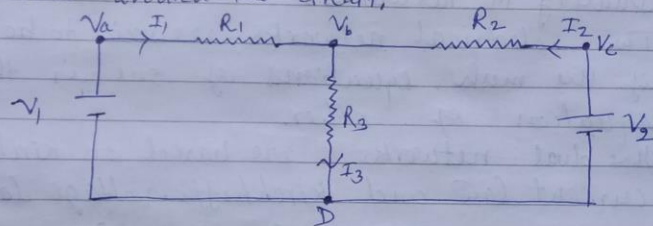Nodal voltage analysis uses the nodal equations of Kirchhoff's first law to find the voltage potentials around the circuit.



In the above circuit, node-D is chosen as the reference node and the other three nodes are assumed to have voltage,  $V_A$ ,  $V_B$  and  $V_C$  with respect to node D.

Now By the Kirchhoff's current law

$$I_1 + I_2 = I_3$$

$$\frac{V_A - V_B}{R_1} + \frac{V_C - V_B}{R_2} = \frac{V_B}{R_3}$$

$$\frac{V_A}{R_1} - \frac{V_B}{R_1} + \frac{V_C}{R_2} - \frac{V_B}{R_2} = \frac{V_B}{R_3}$$

$$\frac{V_A}{R_1} + \frac{V_C}{R_2} = \frac{V_B}{R_1} + \frac{V_B}{R_2} + \frac{V_B}{R_3}$$

$$\frac{V_A}{R_1} + \frac{V_C}{R_2} = V_B \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

(2)

$$V_b \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \left( \frac{V_a}{R_1} + \frac{V_c}{R_2} \right)$$


$$V_b = \frac{\left( \frac{V_a}{R_1} + \frac{V_c}{R_2} \right)}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

if we know the value of  $V_a, V_c, R_1, R_2$  and  $R_3$  then we can easily find the value of  $V_b$ .

\* Duality in networks  $\Rightarrow$

Two electrical networks are said to be dual if the mesh equations of one is the node equation of other.

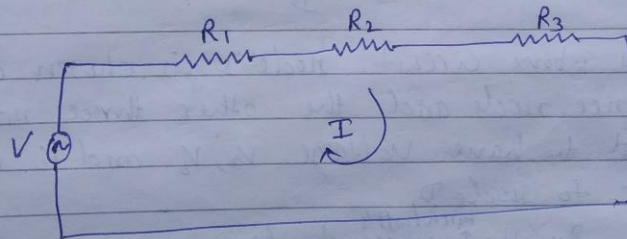The dual networks are based on Kirchhoff's current law and Kirchhoff's voltage law.




Applying Kirchhoff's voltage law in above diagram we get

$$V = IR_1 + IR_2 + IR_3$$

$$V = I(R_1 + R_2 + R_3) \quad \text{--- (1)}$$

(3)

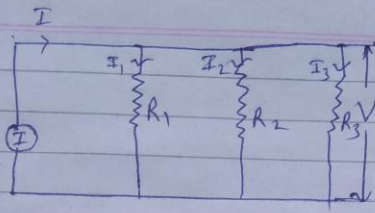

Applying Kirchhoff's current law in above diagram we get.

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \quad \text{--- (2)}$$

we have found two equations (1) and (2) similar in their mathematical form.

Equation (1) is in mesh form and Equation (2) is in nodal form. left side variable in the equation (1) is voltage and left side variable in the equation (2) is current.

Therefore, these two networks are dual networks.

The circuit equations of two dual networks are similar in form but the variables are interchanged.