

Dr. Mohammad Aslam, Dept. of physics.


B.Sc. Part-2, physics (Hons), Paper-IV

Lecture-22.

\* Complex Reactances  $\Rightarrow$

There are two primary types of reactances  $\Rightarrow$

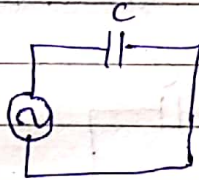① Capacitive reactance  $\rightarrow$  when only capacitor is connected in the circuit.



It is denoted by  $X_C$ .


The complex form of  $X_C$  is

$$X_C = \frac{1}{j\omega C}$$

$$\text{or } X_C = -\frac{j}{\omega C}$$

where  $j$  is complex number,  
 $\omega$  is the angular frequency and  $C$  is the capacitance

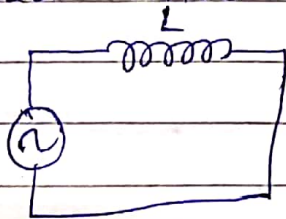② Inductive reactance  $\Rightarrow$  when only inductor is connected with AC circuit.





It is denoted by  $X_L$ .

The complex form of  $X_L$  is

$$X_L = j\omega L, \quad L \text{ is the inductor}$$
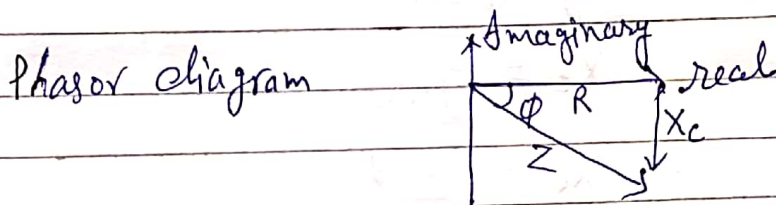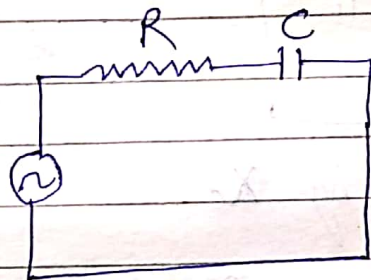
## Complex Impedance $\Rightarrow$

① RC Circuit  $\Rightarrow$  An AC Circuit in which a resistance and a capacitor connected in series.



Now the complex impedance is given as

$$Z = R + X_c$$

$$\text{but } X_c = \frac{-j}{\omega C}$$

$$Z = R - \frac{j}{\omega C}$$

$$\text{or } Z = |Z| e^{j\phi}$$

$$\text{where } |Z| = \sqrt{R^2 + \left(\frac{-1}{\omega C}\right)^2}$$



$$|Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\text{and } \tan \phi = \frac{|X_c|}{|R|} = \frac{1}{\omega R C}$$

$$\tan \phi = \frac{1}{\omega R C}$$

$$\phi = \tan^{-1} \left( \frac{1}{\omega R C} \right)$$

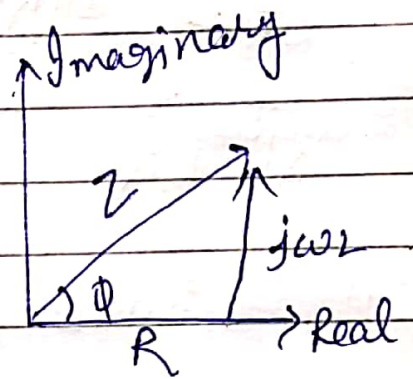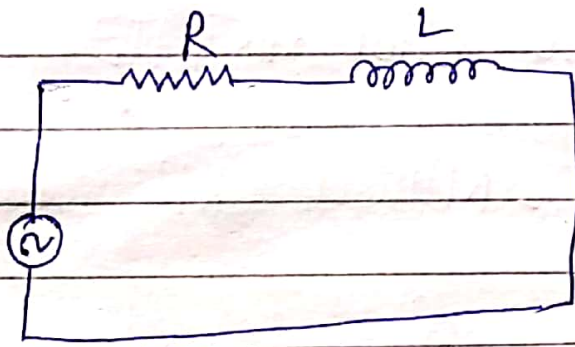② RL Circuit  $\Rightarrow$  An AC circuit in which a resistance and an inductor is connected in series.



The complex impedance is given as

$$Z = R + X_L$$

$$Z = R + j\omega L$$

$$Z = |Z| e^{j\phi}$$

$$|Z| = \sqrt{R^2 + \omega^2 L^2}$$

$$|Z| = \sqrt{R^2 + \omega^2 L^2}$$

$$\tan \phi = \frac{|X_L|}{|R|}$$

$$\tan \phi = \frac{\omega L}{R}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right)$$