

Dr. Mohammad Aslam, Dept.  
Of physics, B.Sc. part-2 physics  
(Hons) paper-iv lecture no-56

## Topic: De Morgan's Theorems

De Morgan has suggested two theorems which are extremely useful in Boolean Algebra. The two theorems are discussed below.

### Theorem 1

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NAND = Bubbled OR

- The left hand side (LHS) of this theorem represents a NAND gate with inputs A and B, whereas the right hand side

(RHS) of the theorem represents an OR gate with inverted inputs.

- ▣ This OR gate is called as **Bubbled OR**.

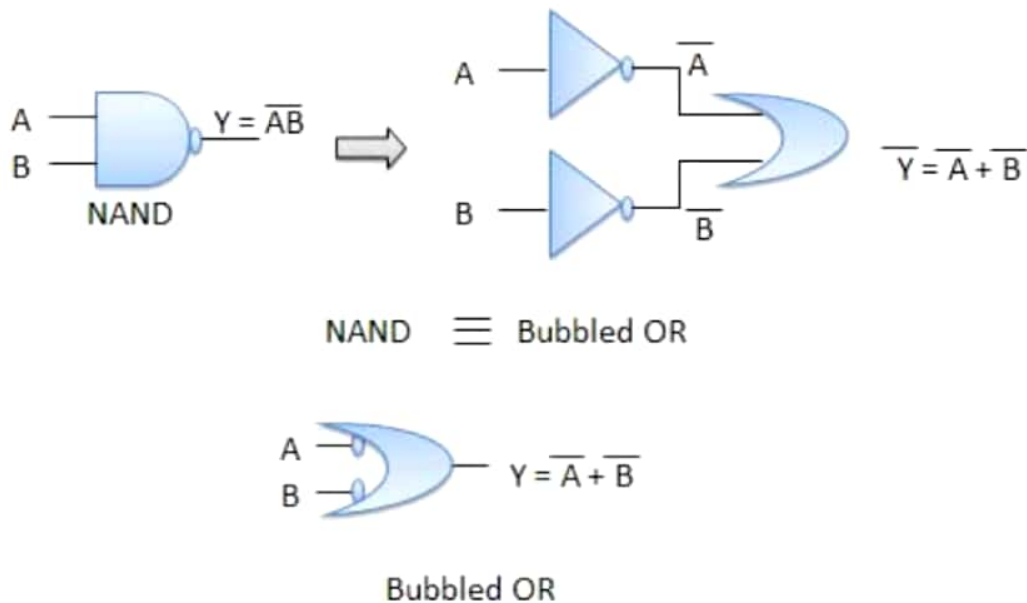


Table showing verification of the De Morgan's first theorem -


A	B	$\overline{AB}$	$\overline{A}$	$\overline{B}$	$\overline{A} + \overline{B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

## Theorem 2


$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

NOR = Bubbled AND

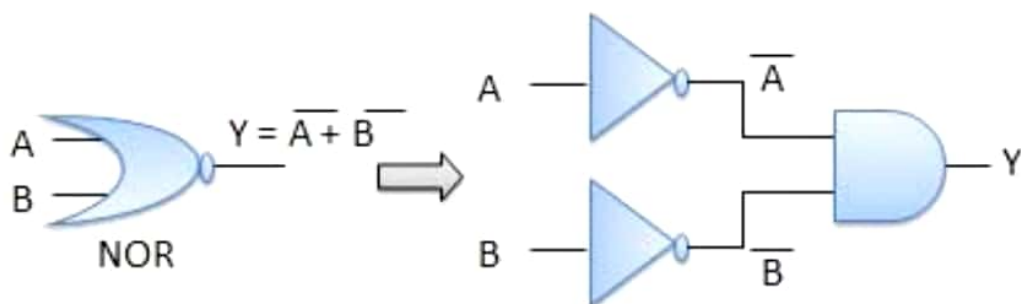- ▣ The LHS of this theorem represents a NOR gate with inputs A and B, whereas the RHS represents an AND gate with inverted inputs.
- ▣ This AND gate is called as **Bubbled AND**.



NOR  $\equiv$  Bubbled AND

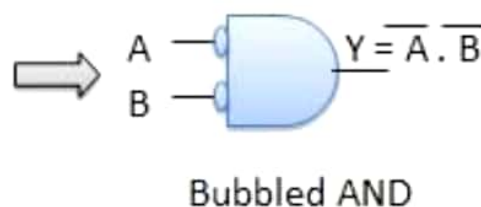

Bubbled AND

Table showing verification of the De Morgan's second theorem -

A	B	$\overline{A+B}$	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0